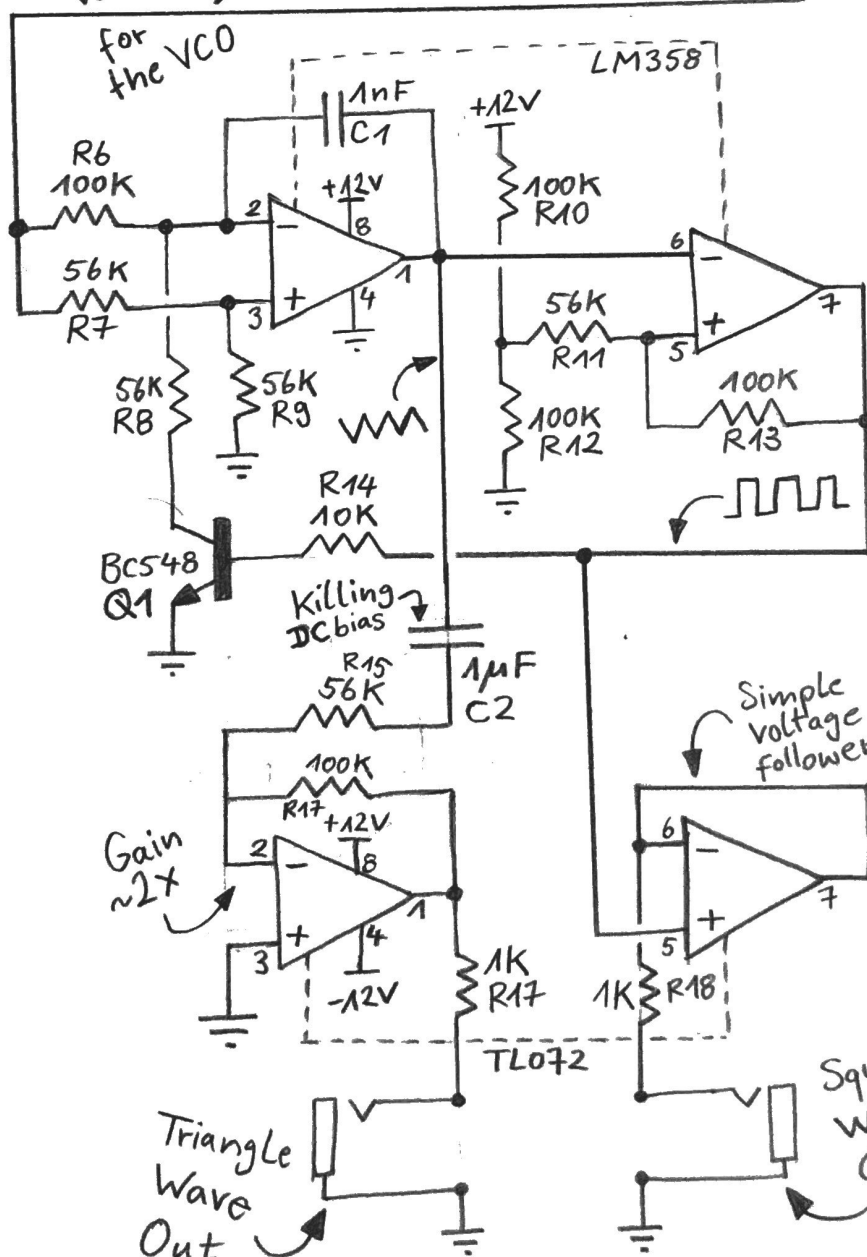


1. Summing the inputs



2. Creating the waves

At this point the triangle has low  $V_{pp}$  and a DC bias.

3. Amplifying everything